

## Formulae for Module 3

### Electrical symbols and units

<i>Quantity</i>	<i>Symbol</i>	<i>Unit</i>	<i>Abbreviated units</i>
Angle	$\phi$	radian or degree	Rad or °
Capacitance	$C$	Farad	F
Charge	$Q$	Coulomb	C
Conductance	$G$	Siemen	S
Current	$I$	Ampere	A
Energy	$J$	Joule	J
Flux	$\Phi$	Weber	Wb
Flux density	$B$	Tesla	T
Frequency	$f$	Hertz	Hz
Impedance	$Z$	Ohm	$\Omega$
Inductance	$L$	Henry	H
Power	$P$	Watt	W
Reactance	$X$	Ohm	$\Omega$
Resistance	$R$	Ohm	$\Omega$
Time	$t$	second	s
Voltage	$V$	Volt	V

### Charge, current and voltage

$$Q = I \times t$$

### Ohm's Law

$$V = I \times R \quad \text{and} \quad I = V / R \quad \text{and} \quad R = V / I$$

Similarly if *resistance* is replaced by *reactance* or *impedance*:

$$\begin{aligned} V &= I \times X & \text{and} & \quad I = V / X & \text{and} & \quad X = V / I \\ V &= I \times Z & \text{and} & \quad I = V / Z & \text{and} & \quad Z = V / I \end{aligned}$$

### Power and energy

$$\begin{aligned} P &= I \times V & \text{and} & \quad P = V^2 / R & \text{and} & \quad P = I^2 R \\ J &= P \times t & \text{and since} & \quad P = I \times V & \text{so} & \quad J = I V t \end{aligned}$$

### Resistors in series

$$R_T = R_1 + R_2 + R_3$$

### Resistors in parallel

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \text{but where there are only two resistors} \quad R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

## Capacitance

$$C = \frac{\epsilon A}{d} \quad \text{where } \epsilon \text{ is the } \textit{permittivity} \text{ of the dielectric and } \epsilon = \epsilon_0 \epsilon_r$$

## Capacitance, charge and voltage

$$Q = C V$$

## Inductance

$$L = n^2 \frac{\mu A}{l} \quad \text{where } \mu \text{ is the } \textit{permeability} \text{ of the magnetic medium and } \mu = \mu_0 \mu_r$$

## Energy stored in a capacitor

$$J = \frac{1}{2} C V^2$$

## Energy stored in an inductor

$$J = \frac{1}{2} L I^2$$

## Inductors in series

$$L_T = L_1 + L_2 + L_3$$

## Inductors in parallel

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \quad \text{but where there are } \textit{only} \text{ two inductors } L_T = \frac{L_1 \times L_2}{L_1 + L_2}$$

## Capacitors in series

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad \text{but where there are } \textit{only} \text{ two capacitors } C_T = \frac{C_1 \times C_2}{C_1 + C_2}$$

## Capacitors in parallel

$$C_T = C_1 + C_2 + C_3$$

## Induced e.m.f. in an inductor

$$e = -L \frac{di}{dt} \quad \text{where } \frac{di}{dt} \text{ is the } \textit{rate of change of current with time}$$

## Current in a capacitor

$$i = C \frac{dv}{dt} \quad \text{where } \frac{dv}{dt} \text{ is the } \textit{rate of change of voltage with time}$$

## Sine wave voltage

$$v = V_{\max} \sin(\omega t) \quad \text{or} \quad v = V_{\max} \sin(2\pi f t) \quad \text{because} \quad \omega = 2\pi f$$

$$f = 1/T \quad \text{where } T \text{ is the periodic time}$$

For a *sine wave*, to convert:  
**RMS to peak** multiply by **1.414**  
**Peak to RMS** multiply by **0.707**  
**Peak to average** multiply by **0.636**  
**Peak to peak-peak** multiply by **2**

## Capacitive reactance

$$X_C = \frac{V_C}{I_C} = \frac{1}{2\pi f C}$$

## Inductive reactance

$$X_L = \frac{V_L}{I_L} = 2\pi f L$$

## Resistance and reactance in series

$$Z = \sqrt{(R^2 + X^2)} \quad \text{and} \quad \phi = \arctan\left(\frac{X}{R}\right)$$

## Resonance

$$X_L = X_C \quad \text{thus} \quad \omega L = \frac{1}{\omega C} \quad \text{or} \quad 2\pi f_o L = \frac{1}{2\pi f_o C}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

## Power factor

Power factor = True power/Apparent power = Watts / Volt-amperes = W / VA

$$\text{True power} = V \times (I \times \cos \phi) = VI \cos \phi \quad \text{Power factor} = \cos \phi = R/Z$$

$$\text{Reactive power} = V \times (I \times \sin \phi) = VI \sin \phi$$

## Motors and generators

$$F = BIl$$

$$f = pn / 60 \quad \text{where } p \text{ is the number of pole pairs and } n \text{ is the speed in r.p.m.}$$

## Three phase

$$\text{Star connection} \quad V_L = 1.732 \times V_P \quad \text{and} \quad I_L = I_P \quad \text{note that } 1.732 = \sqrt{3}$$

$$\text{Delta connection} \quad V_L = V_P \quad \text{and} \quad I_L = 1.732 \times I_P$$

$$\text{Power in a three phase load} \quad P = 3 \times V_P I_P \cos \phi = 1.732 \times V_L I_L \cos \phi$$